

1 Logic Circuits

A **logic circuit** (or **digital circuit**) receives input signals p_1, p_2, \dots, p_n , each a bit, and produces output signals s_1, s_2, \dots, s_n , each a bit.

